

**Bago University**  
**Department of Physics**  
**First Semester Examination, March 2019**

**Fourth Year (BSc)**  
**(Physics Specialization)**


**Phys 4101**  
**Electronics**  
**Time Allowed: (3) Hours**

Answer any Six questions.

- 1 (a) What do you understand by the terms: (i) class A amplifier, (ii) class B amplifier and (iii) class C amplifier? Draw the circuit diagram of a tuned class C amplifier.
- (b) What are the maximum peak value of collector current and output voltage of the class A amplifier expressed below? Also find the large signal voltage gain and power gain of the amplifier. The component values of the amplifier are:  
 $R_1 = 12 \text{ k}\Omega$ ,  $R_2 = 3.3 \text{ k}\Omega$ ,  $R_C = 1.2 \text{ k}\Omega$ ,  $R_E = 330 \Omega$ ,  $R_L = 12 \text{ k}\Omega$ ,  $V_{CC} = +9\text{V}$ ,  $\beta = 150$ ,  $\beta_{dc} = 200$ . Assume that  $r_e' = 7 \Omega$ .


- 2 (a) (i) What is the class B push-pull amplifier?  
(ii) What is the resonant frequency of a tank circuit with  $L = 10\text{mH}$  and  $C = 0.001\mu\text{F}$ ?
- (b) A class C amplifier is driven by a 200kHz signal. The transistor is on for  $1\mu\text{s}$ , and the amplifier is operating over 100 percent of its load line. If  $I_{C(sat)} = 100\text{mA}$  and  $V_{CE(sat)} = 0.2\text{V}$ .  $V_{CC}$  equal to 24V and the  $R_C$  is  $100\Omega$ . What is the average power dissipation and determine the efficiency?

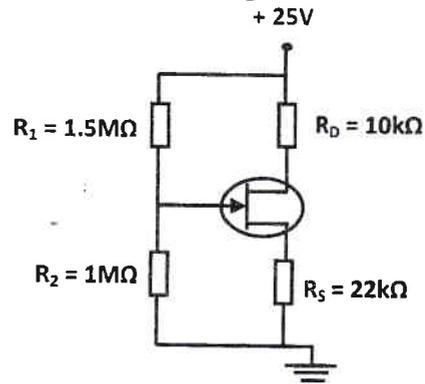- 3 (a) Derive the ac voltage gain of common source amplifier with voltage divider bias.  
(b) What is the drain voltage in following figure?  
Draw also the dc load line and Q-point for following figure.



- 4 (a) Drawing the equivalent circuit, find the voltage gain of a source follower FET amplifier with voltage divider bias.  
(b) Draw the circuit diagram of a common source FET amplifier with voltage divider bias using the following components.  
 $R_1 = 20 \text{ M}\Omega$ ,  $R_2 = 10 \text{ M}\Omega$ ,  $R_D = 1 \text{ k}\Omega$ ,  $R_S = 2 \text{ k}\Omega$  and  $g_m = 2000 \mu\text{S}$ .  
What will be the voltage gain of the circuit? Also express the voltage gain in decibel. If 2 mV signal is applied to the amplifier, what will be the output voltage?
- 5 (a) List the capacitances that affect low-frequency gain of a bipolar amplifier. Also list the capacitances that affect high-frequency gain.  
(b) The component values of bipolar transistor amplifier are given below. Find the critical frequency and phase shift due to (i) input coupling capacitor  $C_1$  and (ii) output coupling capacitor  $C_2$ .  
 $R_S = 1 \text{ k}\Omega$ ,  $C_1 = 0.1 \mu\text{F}$ ,  $R_1 = 60 \text{ k}\Omega$ ,  $R_2 = 20 \text{ k}\Omega$ ,  $V_{CC} = 10 \text{ V}$ ,  $R_C = 2 \text{ k}\Omega$ ,  
 $R_E = 1 \text{ k}\Omega$ ,  $C_2 = 0.1 \mu\text{F}$ ,  $C_3 = 10 \mu\text{F}$ ,  $R_L = 10 \text{ k}\Omega$ ,  $\beta = 100$ ,  $r_e' = 13.9 \Omega$ .

- 6 (a) What are the effect of coupling capacitors and bypass capacitor at lower frequencies?  
 (b) For an output RC circuit in a certain amplifier,  $R_C = 10\text{k}\Omega$ ,  $C_2 = 0.1\mu\text{F}$  and  $R_L = 10\text{k}\Omega$ .  
 (i) Determine the critical frequency.  
 (ii) If the midrange voltage gain of the amplifier is 50, what is the gain at the critical frequency?
- 7 (a) Compare a practical op-amp to the ideal op-amp.  
 Define the differential input impedance of an op-amp.  
 (b) Determine the voltage gain of the amplifier in dB. If  $V_{in} = 0.5\text{V}$ , what will be the value of  $V_f$ ?  
 The open-loop voltage gain is 100000. If the CMRR of the op-amp is 80 dB, what will be the common-mode gain of this op-amp?

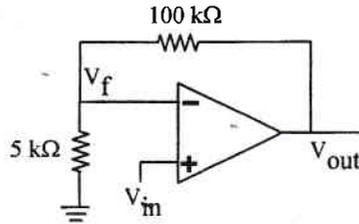

- 8 (a) Derive output impedance of the noninverting amplifier with circuit diagram.  
 (b) (i) Determine the input and output impedances of the amplifier in Figure. The op-amp sheet gives  $Z_{in} = 2\text{M}\Omega$ ,  $Z_{out} = 75\Omega$  and  $A_{ol} = 200000$ . (ii) Find the closed-loop voltage gain.

